

Salida A

		<i>AB</i>			
		00	01	11	10
<i>CD</i>	00	1	0	0	1
	01	1	1	1	0
	11	0	0	0	0
	10	0	1	1	1

Salida B

		<i>AB</i>			
		00	01	11	10
<i>CD</i>	00	1	0	1	1
	01	1	1	0	1
	11	0	0	0	0
	10	0	1	1	1

		<i>AB</i>			
		00	01	11	10
<i>CD</i>	00	1	0	1	1
	01	0	1	1	1
	11	0	0	0	0
	10	1	1	1	1

Salida C

		<i>AB</i>			
		00	01	11	10
<i>CD</i>	00	1	0	0	1
	01	1	1	1	0
	11	0	0	0	0
	10	1	0	0	1

Salida D

		<i>AB</i>			
		00	01	11	10
<i>CD</i>	00	1	0	0	1
	01	1	1	1	0
	11	0	0	0	0
	10	1	0	0	1

Salida E

		<i>AB</i>			
		00	01	11	10
<i>CD</i>	00	1	0	0	1
	01	0	0	1	1
	11	0	0	0	0
	10	1	0	1	1

Salida F

		<i>AB</i>			
		00	01	11	10
<i>CD</i>	00	1	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	1	0	1	1

Salida G